

Roll No.,

Total No. of Questions : 05]

[Total No. of Printed Pages : 02

EYS-163

B. Tech. (New Scheme) Examination, 2024

(Fourth Semester)

ANALOG CIRCUITS

EL-402

Time : 3 Hours]

[Maximum Marks : 60

Note : Attempt all questions. All questions carry equal marks.

1. Discuss Biasing Schemes for BJT and FET Amplifier with diagram.

Or

Explain the following :

- (a) Voltage amplifier
 - (b) Current amplifier
 - (c) Trans-resistance amplifier.
2. Draw and explain frequency response of single stage and multistage amplifiers.

(2-M24-12/23) N-EYS-163

P.T.O.

Or

Explain various classes of amplifier with diagram.

3. Explain the following :
 - (a) RC Oscillators
 - (b) Phase shift oscillator
 - (c) Wien bridge oscillator.

Or

Explain differential amplifier and its operation.

4. Draw and explain the operation of precision rectifier using op-amp.

Or

Explain different parameters of op-amp.

5. Explain weighted resistor digital to analog converters.

Or

Explain single slope and dual slope analog to digital converters.